

Lecture 7

# INDUCTORS

---

Maha K. Omar

# INDUCTORS

---

- ✖ Faraday's Law states that: the magnitude of the induced voltage in a circuit is proportional to the rate of change of the flux passing through the circuit.
- ✖ Lenz's Law: the polarity of the induced voltage is such as to oppose the cause producing it.
- ✖ Counter emf or back voltage: the induced voltage that tries to opposes changes in current. This voltage does not stop the current from changing. It only stops sudden changes .

# INDUCTORS

- ✖ The induced voltage depends on the coil core. Ferromagnetic cores confine the flux entirely. They are called iron-core coils. Nonmagnetic cores have same permeability as air and do not confine flux. They are called air core coils.
- ✖ For iron-core, the induced emf is given by:

$$e = N \frac{d\phi}{dt}$$

Where Flux  $\phi$  lines are passing through N turns.

# INDUCTORS

- ✖ For air core inductors, the induced emf is proportional to the rate of current change:

$$e = L \frac{dI}{dt}$$

Where L is the self inductance.

- ❖ Inductances in series will have a total inductance of

$$L_{tot} = L_1 + L_2 + L_3 + \dots$$


- ❖ Inductance in parallel will have a total inductance of

$$\frac{1}{L_{tot}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots$$



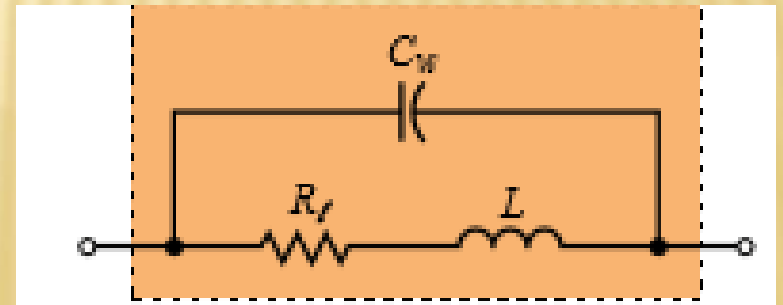
# STRAY CAPACITANCE AND INDUCTANCE

- ✖ Coil resistance: since inductors are made up of imperfect conductors, they also resistance. This is usually graphed as a resistance in series.
- ✖ Stray capacitance for an inductor coil: it is produced because the inductor turns are separated from each other by insulation.
- ✖ Stray inductance: it is due to magnetic effects of electric current. All current carrying have inductance.



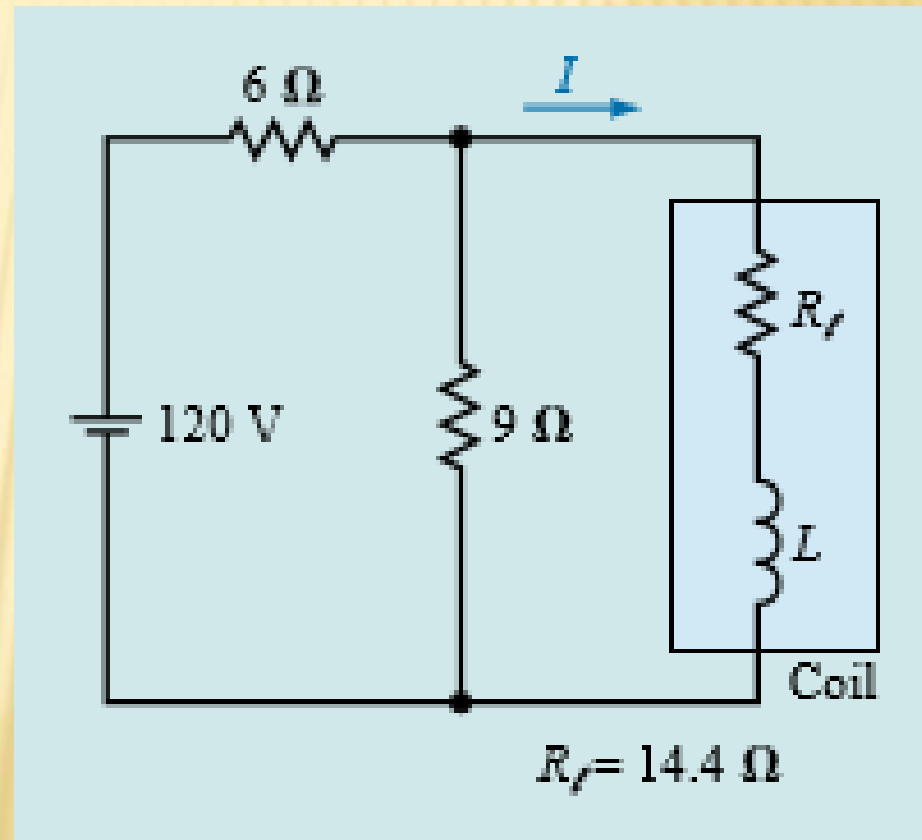
# PROBLEM

- ✖ The coil resistance is  $14.4$ . what is the steady state current?


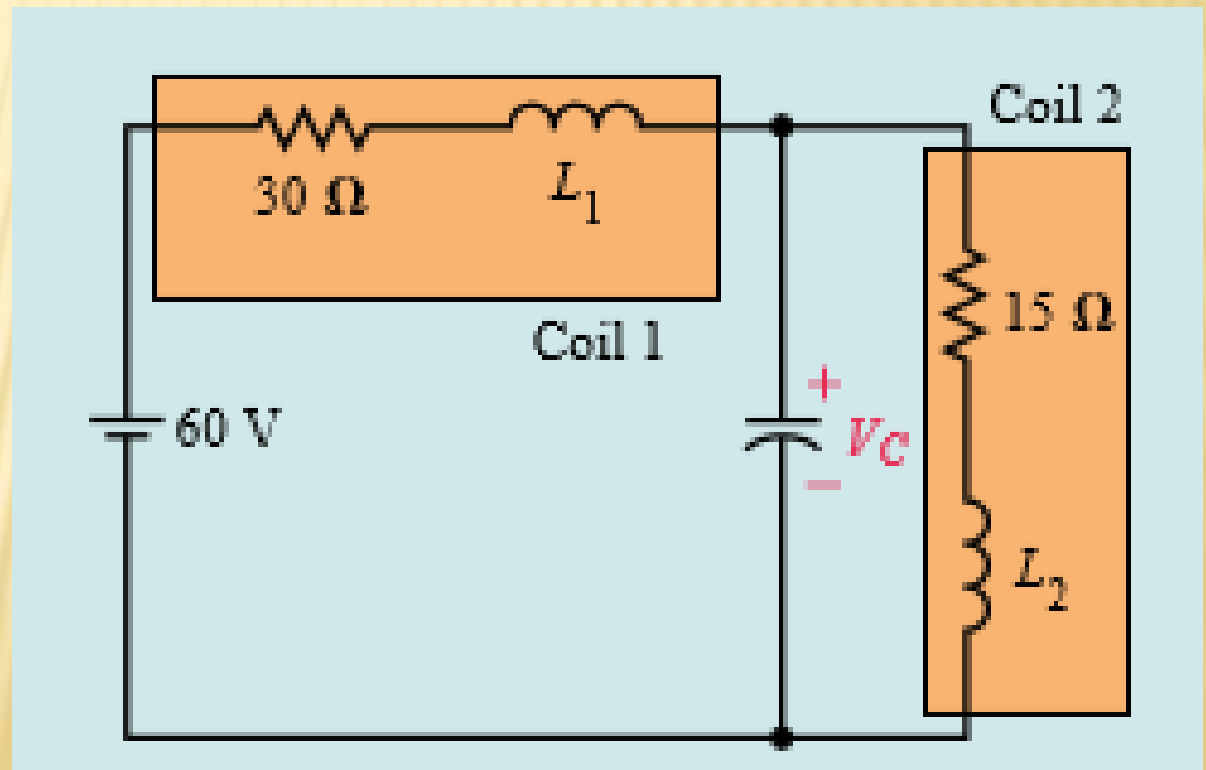
# PROBLEM

- ✖ The resistance of coil 1 is 30 and that of coil 2 is 15. Find the voltage across the capacitor assuming steady state dc?



# ENERGY STORED

- ✖ Energy stored by an inductance

$$P = IV \Rightarrow W = \int P dt$$

$$W = \int IV dt = \int IL \frac{dI}{dt} dt = \int IL dI = \frac{1}{2} LI^2$$

- ✖ Energy stored by a capacitance


$$P = IV \Rightarrow W = \int P dt$$

$$W = \int IV dt = \int VC \frac{dV}{dt} dt = \int CV dV = \frac{1}{2} CV^2$$





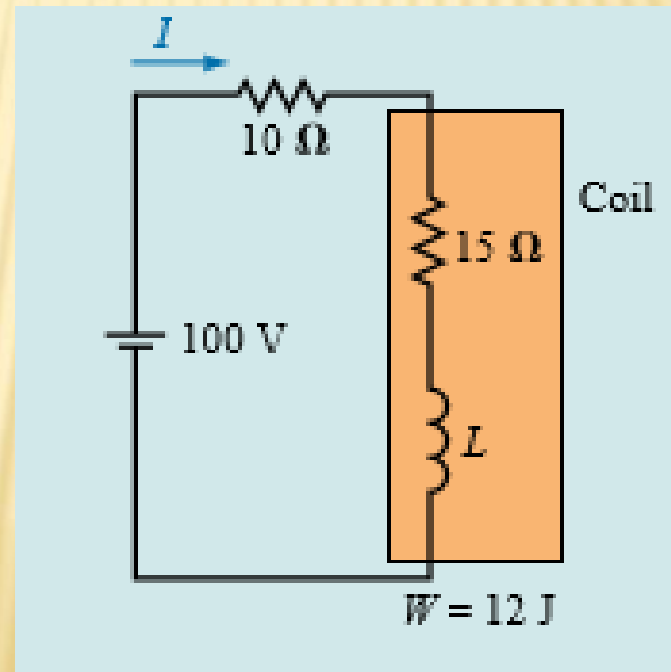
# PROBLEM

- ✗ The coil has a resistance of  $15\ \Omega$ . when the current reaches its steady state value, the energy stored is  $12\text{ J}$ . what is  $L$ ?


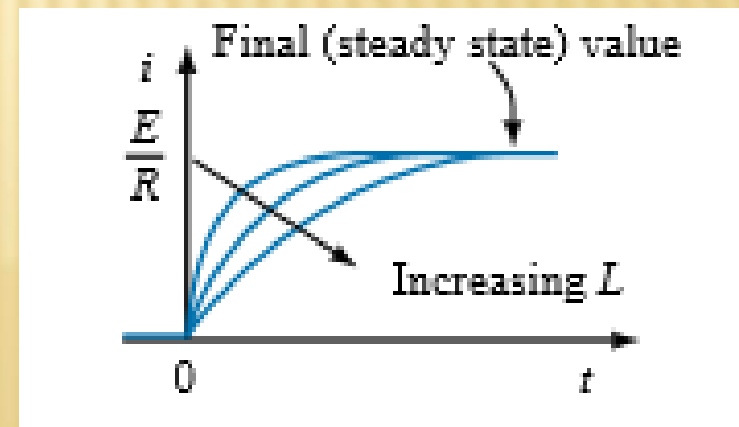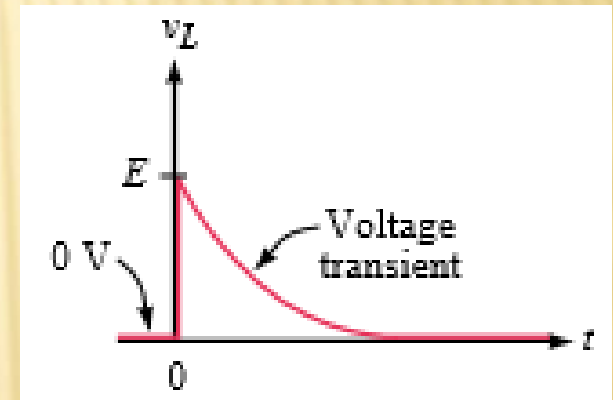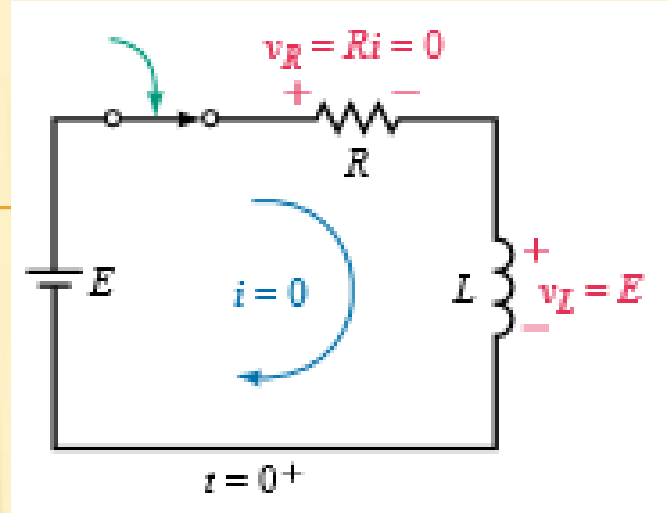
# INDUCTANCE ENERGIZING

- ✗ When the switch is closed, induced back emf is produced. The voltage will decay to zero as the current reaches steady state.
- ✗ For the current, it starts building up from zero.



# INDUCTOR ENERGIZING

$$V_L + V_R = E \Rightarrow V_L + IR = E$$

$$V_L = L \frac{dI}{dt} \Rightarrow L \frac{dI}{dt} + IR = E$$

$$\frac{dI}{dt} = -\frac{R}{L} \left( I - \frac{E}{R} \right)$$

$$\frac{dI}{I - E/R} = -\frac{Rdt}{L}$$

$$\int_0^I \frac{dI}{I - E/R} = -\int_0^t \frac{Rdt}{L}$$

$$\ln(I - E/R) - \ln(-E/R) = -\frac{Rt}{L}$$

$$\ln\left(\frac{IR - E}{-E}\right) = -\frac{Rt}{L}$$

$$-\frac{IR}{E} + 1 = e^{-\frac{Rt}{L}}$$



$$I = \frac{E}{R} (1 - e^{-Rt/L})$$

$$V_R = IR = E(1 - e^{-Rt/L})$$

$$V_L = E - V_R = Ee^{-Rt/L}$$
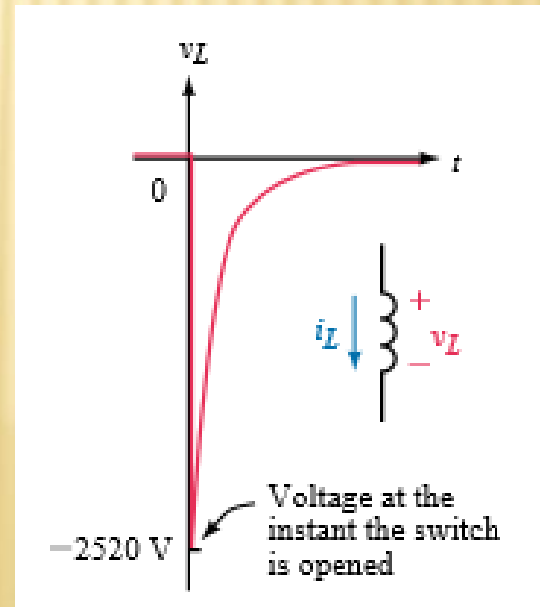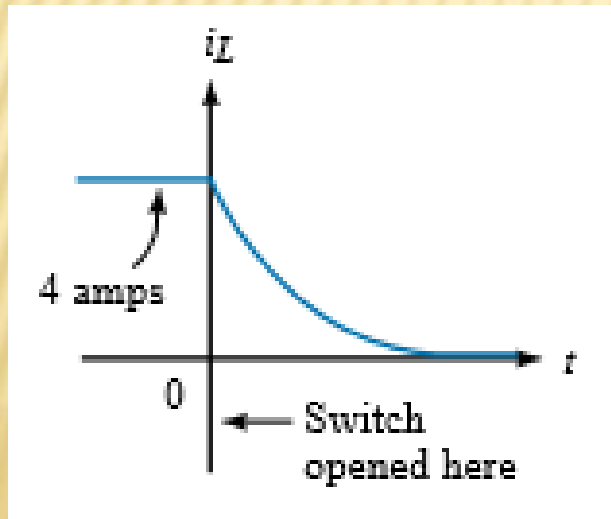
# DE ENERGIZING CASE

- ✗ In this case, the current going through the inductance has an original value so the induced emf will have an opposite sign to before. It will gradually decay to zero again.
- ✗ The current, on the other hand, will decay gradually to zero.





# INDUCTOR DE-ENERGIZING

$$V_L + V_R = 0 \Rightarrow V_L + IR = 0$$

$$V_L = L \frac{dI}{dt} \Rightarrow L \frac{dI}{dt} + IR = 0$$

$$\frac{dI}{dt} = -\frac{R}{L} I$$

$$\frac{dI}{I} = -\frac{Rdt}{L}$$

$$\int_{I_0}^I \frac{dI}{I} = -\int_0^t \frac{Rdt}{L}$$

$$\ln(I) - \ln(I_0) = -\frac{Rt}{L}$$

$$\ln\left(\frac{I}{I_0}\right) = -\frac{Rt}{L}$$

$$\frac{I}{I_0} = e^{-\frac{Rt}{L}}$$

$$I = I_0 e^{-Rt/L} = \frac{E}{R} e^{-Rt/L}$$

$$V_R = IR = E e^{-Rt/L}$$


$$V_L = L \frac{dI}{dt} = -\frac{E}{L} e^{-Rt/L}$$

# TIME CONSTANT & DURATION OF A TRANSIENT

- ✘ The time constant  $T=L/R$  and it determines the rate at which inductor energize or de-energize.
- ✘ The transient time depends on the exponential function. 99.3% of the transient takes place in the first  $5T$  seconds.


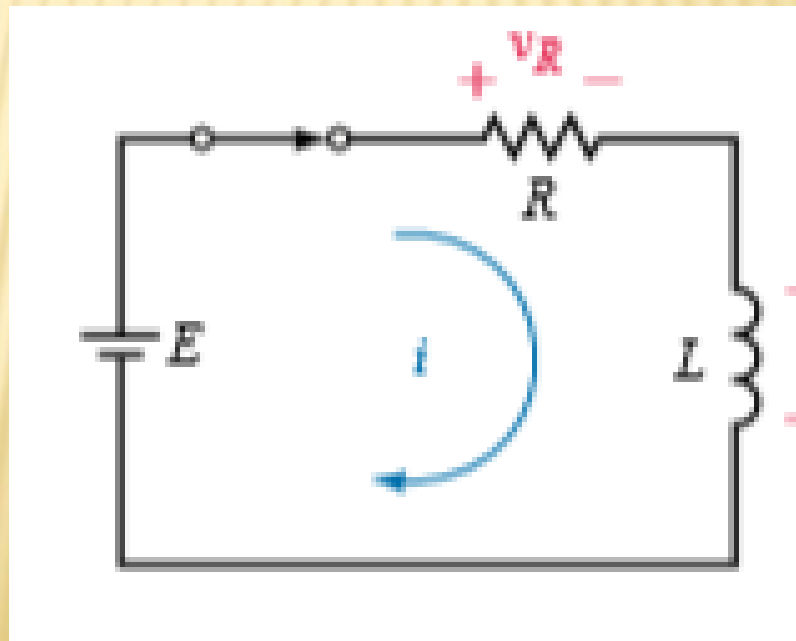
# PROBLEM

- ✗ If  $E=50\text{ V}$ ,  $R=10\Omega$ , and  $L=2\text{H}$  and it is in the energizing stage, find:
  1. Expression for  $V_L$  and  $I_L$
  2. Plot the relations for  $V_L$ ,  $I_L$ ,  $V_R$
  3. What is the steady state current?


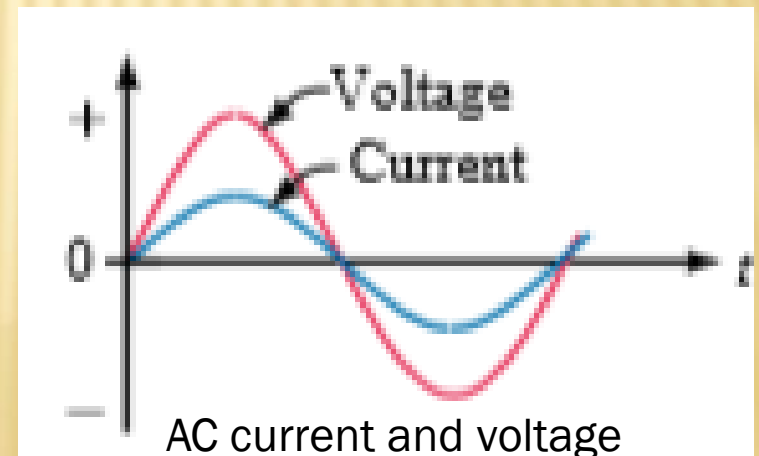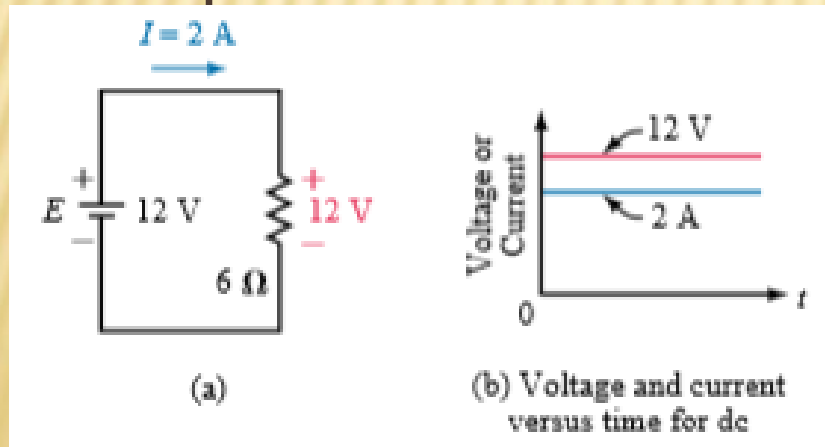
# DC VERSUS AC SOURCES


- ✗ DC sources have constant magnitude and polarity while as AC sources changes both magnitude and polarity.
- ✗ The common ac sources used in our daily life take the form of sinusoidal change (the shape of a sine wave).





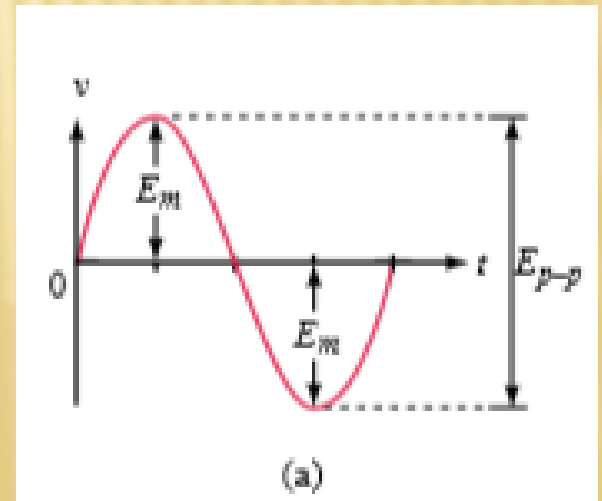
# FREQUENCY, PERIOD, AMPLITUDE AND PEAK

- ✗ The frequency ( $f$ ) of the waveform is the number of cycles per second and it measured in Hertz (Hz).
- ✗ The period ( $T$ ) is the duration of one cycle or the inverse of the frequency  $T=1/f$ .
- ✗ The amplitude ( $V_m, I_m$ ) is the distance from its average to its peak.
- ✗ Peak to Peak ( $V_{p-p}, I_{p-p}$ ) is measured between minimum and maximum peaks.
- ✗ The angular velocity or angular frequency ( $\omega=2\pi f=2\pi/T$ ).



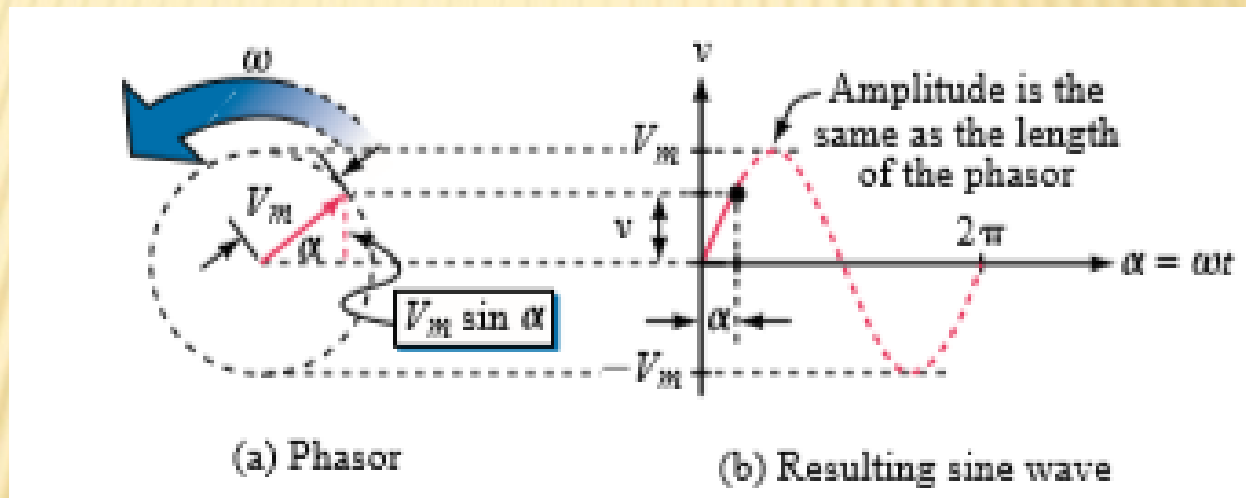
# PHASORS

- ✖ The phasor is a rotating line whose projection on a vertical axis can be used to represent sinusoidal varying quantities.



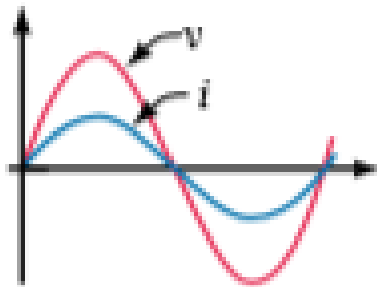
# PHASE DIFFERENCE


- ✗ The angular displacement between different waveforms of the same frequency.
- ✗ If the angular displacement is 0, they are in phase otherwise they are out of phase.



(a) In phase

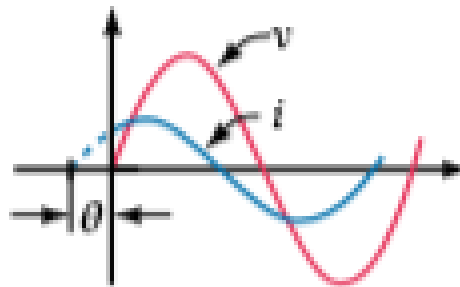

(b) Current leads

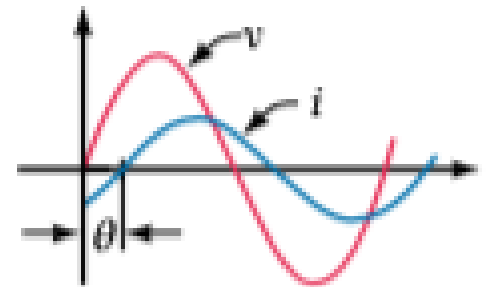

(c) Current lags

# PROBLEM

---

- ✖ If  $V=20 \sin(\omega t+30^\circ)$  and  $i=18 \sin(\omega t-40^\circ)$ , draw the waveforms and determine phase relationships.